

University of Southern California

Viterbi School of Engineering

EE352

Computer Organization and Architecture

HW Constructs

References:

- 1) Textbook
- 2) Mark Redekopp's slide series

Shahin Nazarian





Spring 2010

Logic Circuits

- Combinational logic
 - Perform a specific function (mapping of 2^n input combinations to desired output combinations)
 - No internal state or feedback
 - Given a set of inputs, we will always get the same output after some time (propagation) delay
- Sequential logic (“Storage” devices)
 - Registers made up of flip-flops/latches are the fundamental building blocks
 - Controlled by a “clock” signal
 - Sample data on a “clock” edge and remember that value until the next edge


Transistor Review

    - 3-terminal device
 - Gate input: the control input; its voltage determines whether current can flow
 - Source & Drain: terminals that current flows from/to




Fundamental Blocks: Logic Gates

 - All digital circuits are built from transistors (voltage controlled switches) which can be on or off
- The arrangement of transistors leads to a few basic functions that express logical operations
 - These constructs are known as gates




Transistors in SERIES = AND

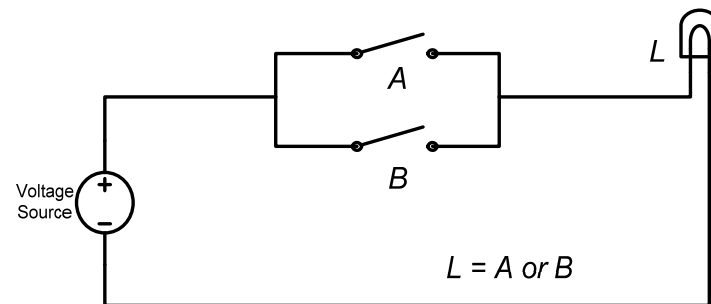


Transistors in PARALLEL = OR

AND Gates

 - An AND gate outputs a '1' (true) if ALL inputs are '1' (true)
- Gates can have several inputs
- Behavior can be shown in a truth table (listing all possible input combinations and the corresponding output)




2-input AND

 


3-input AND

OR Gates

 - An OR gate outputs a '1' (true) if ANY input is '1' (true)
- Gates can also have several inputs




2-input OR

 



3-input OR

NOT Gate

 - A NOT gate outputs a '1' (true) if the input is '0' (false)




NAND and NOR Gates

  

$$Z = \overline{X \cdot Y}$$

X	Y	Z
0	0	0
0	1	0
1	0	0
1	1	1



AND

 

X	Y	Z
0	0	1
0	1	1
1	0	1
1	1	0

NAND


True if NOT ALL
inputs are true

  

$$Z = \overline{X + Y}$$

X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	1

OR

 


X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	0

NOR

True if NOT ANY
input is true

XOR and XNOR Gates

 


XOR

$$Z = X \oplus Y$$

X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	0

 True if an **odd** # of inputs are true
= True if inputs are **different**



XNOR


$$Z = \overline{X \oplus Y}$$

X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	1

True if an **even** # of inputs are true
= True if inputs are **same**

Logic Functions

 - Map input combinations of n -bits to desired m -bit output
- Can describe function with a truth table and then find its circuit implementation





IN0	IN1	IN2	OUT0	OUT1
0	0	0	0	1
0	0	1	1	1
	...			
1	1	1	0	0

Functions & Logic Networks

- We can generate arbitrary logic functions using multiple levels of logic
- Ex: Full Adder performs one column of addition of two numbers
- Adds a bit from each number plus a carry-in from the previous column and generates a sum bit & carry-out


X	Y	C _{in}	C _{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

  

Functions & Logic Networks

- Find patterns in the input combinations that uniquely identify the rows where the output is 1.


X	Y	C_i	C_o
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

 

Functions & Logic Networks

- Decompose function into smaller sub-functions that can easily be implemented. Then recombine sub-functions to create overall function


X	Y	C_i	C_o	$X \cdot Y$	$X \cdot C_i$	$Y \cdot C_i$
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	0
0	1	1	1	0	0	1
1	0	0	0	0	0	0
1	0	1	1	0	1	0
1	1	0	1	1	0	0
1	1	1	1	1	1	1

 

Functions & Logic Networks

- Functions with multiple outputs can be generated by considering each output as a separate function of the inputs
- Example: A dedicated 4-bit adder
 
$$\begin{array}{rcl} & A_3 A_2 A_1 A_0 & = A \\ + & B_3 B_2 B_1 B_0 & = B \\ \hline S_4 S_3 S_2 S_1 S_0 & = S \end{array}$$




Combinational Functional Blocks

- We can take our logic gates and build up a set of commonly used functional blocks
- For this class, the common functional blocks include
 - Adders
 - Multiplexers
 - ALU (Arithmetic and Logic Units)


Adders

 - Take two numbers as input and produce the binary sum




Multiplexers

 
- Along with adders, multiplexers are most used building block
- n data inputs, $\log_2 n$ select bits, 1 output
- A **multiplexer** (“mux” for short) selects one data input and passes it to the output




Multiplexers

 

Multiplexers


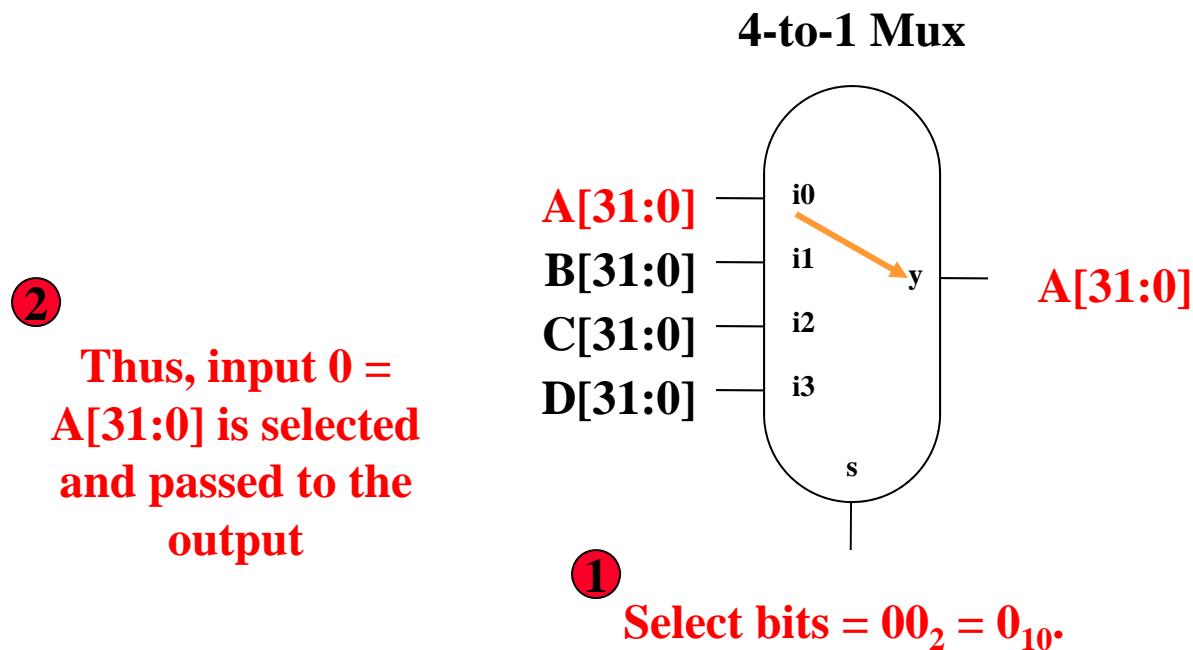


Multiplexers

 


Building a Mux

  - To build a mux
 - Decode the select bits and include the corresponding data input
 - Finally OR all the first level outputs together




Building a Mux

 - To build a mux
 - Decode the select bits and include the corresponding data input
 - Finally OR all the first level outputs together




Building a Mux

 - To build a mux
 - Decode the select bits and include the corresponding data input
 - Finally OR all the first level outputs together



ALU's

 
- Perform a selected operation on two input numbers
 - FS[5:0] select the desired operation



Func. Code	Op.	Func. Code	Op.
00_0000	A SLL B	10_0000	A+B
00_0010	A SRL B	10_0010	A-B
00_0011	A SRA B
...	...	10_0100	A AND B
01_1000	A * B	10_0101	A OR B
01_1001	A * B (uns.)	10_0110	A XOR B
01_1010	A / B	10_0111	A NOR B
01_1011	A / B (uns.)
...	...	10_1010	A SLT B

Simple ALU Design

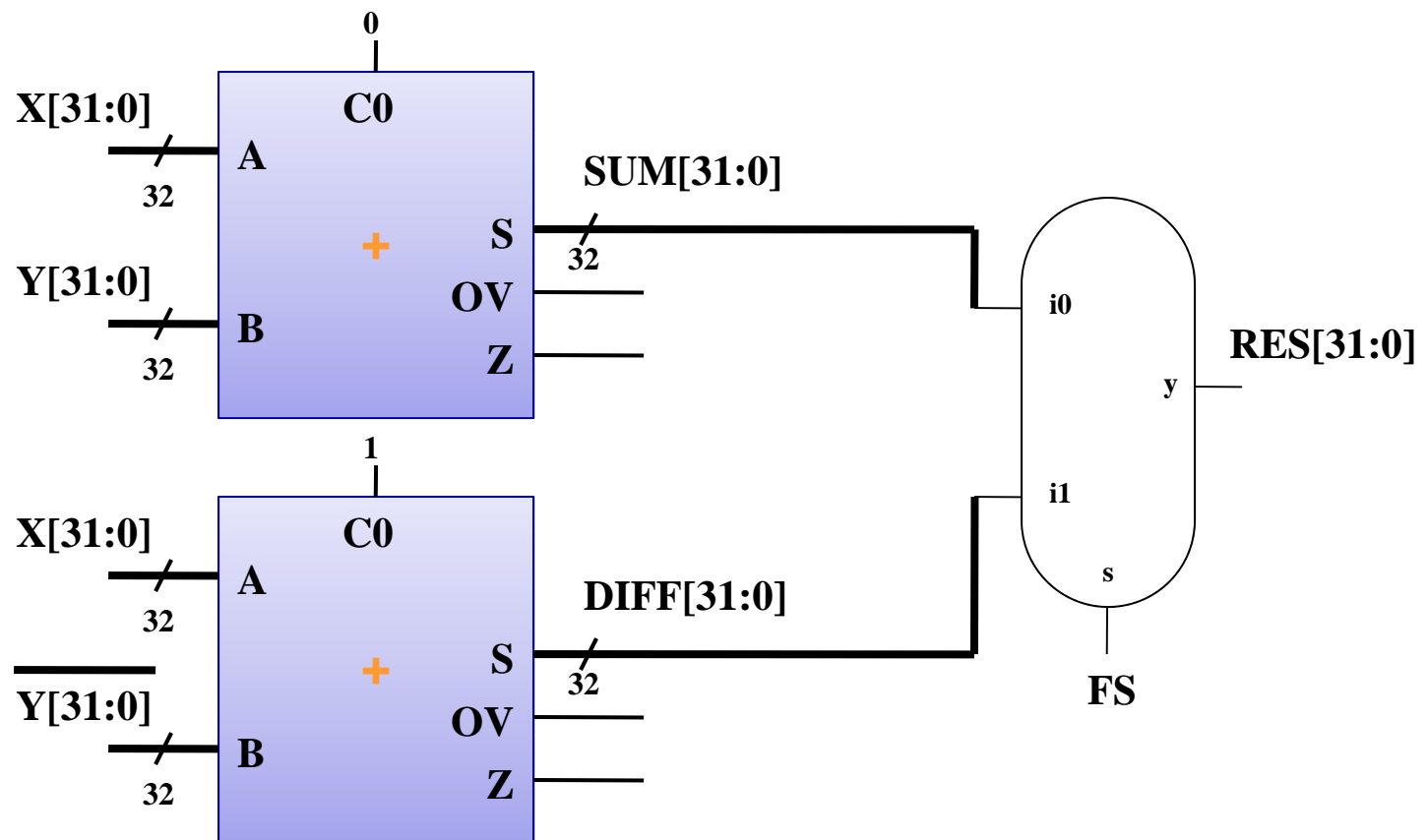
- Build an ALU to either ADD or SUB X and Y, based on an input FS (0=Add, 1=Sub)




Delay in Combinational Logic

- Beyond the functionality, it is important to understand the timing of logic circuits
- Each gate (transistor) has inherent propagation delay
 - Propagation Delay = time from the instant the inputs change until the output becomes stable and correct
- Delay of a circuit is proportional to the longest path (chain) of gates from any input to the output

Delay Example

 


Delay Example

 

**Change in V, B, or T must propagate
through the 4 levels of logic**


Delay Example

 

**Change P must propagate
through only 2 levels of logic**

Timing Example

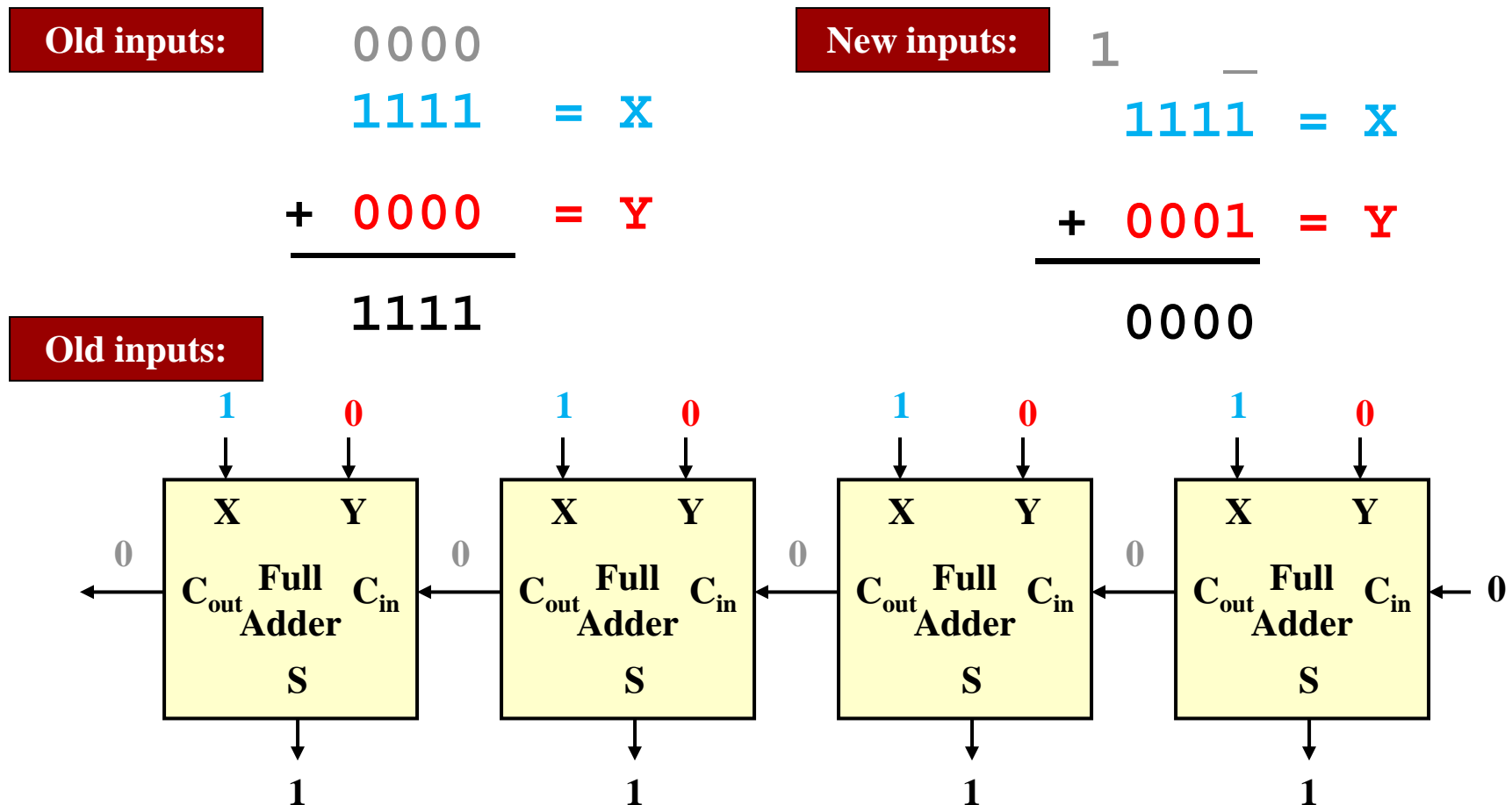- Assume that we were adding one set of inputs and then change to a new set of inputs:



Timing

- At the time just before we enter the new input values, all carries are 0's

New inputs:

$$\begin{array}{r} 1 \quad \text{---} \\ 1111 = X \end{array}$$


$$+ 0001 = Y$$

$$\hline 0000$$

Time

0

Old inputs:

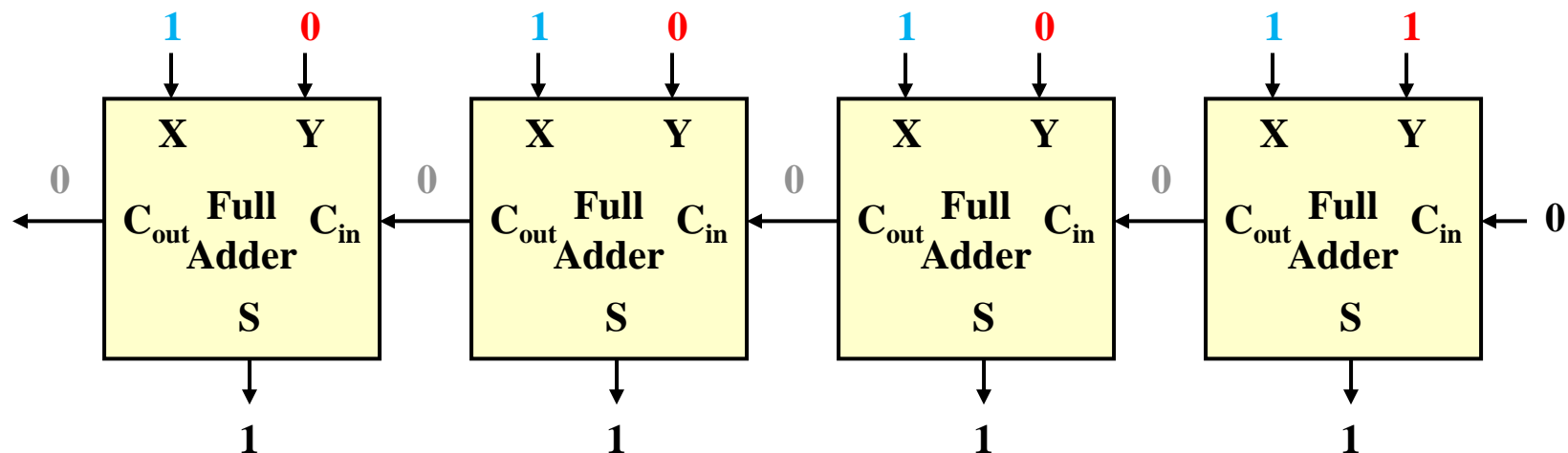

Timing


- The first adder updates his carry and sum but meanwhile other adders output "incorrect" values due to the lack of correct carries

New inputs:

$$\begin{array}{r}
 1 \quad \text{---} \\
 1111 = X \\
 + 0001 = Y \\
 \hline
 0000
 \end{array}$$

Time
1

Old inputs:

 

Timing

- The second adder updates his carry and sum but later adders are still incorrect

New inputs:

$$\begin{array}{r} 1 \quad _ \\ 1111 = X \end{array}$$


$$+ \quad 0001 = Y$$

$$\hline 0000$$

Time

2

Old inputs:

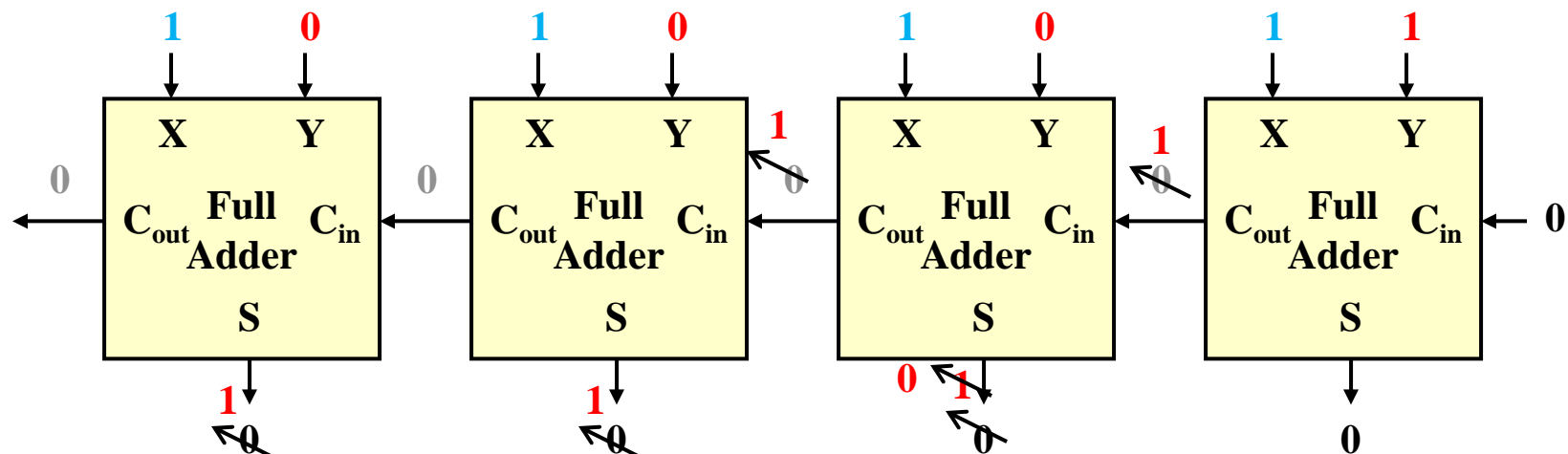

Timing

- The third adder is now correct but the last adder is still incorrect

New inputs:

$$\begin{array}{r} 1 \quad _ \\ 1111 = X \end{array}$$


$$+ 0001 = Y$$

0000

Time

3

Old inputs:

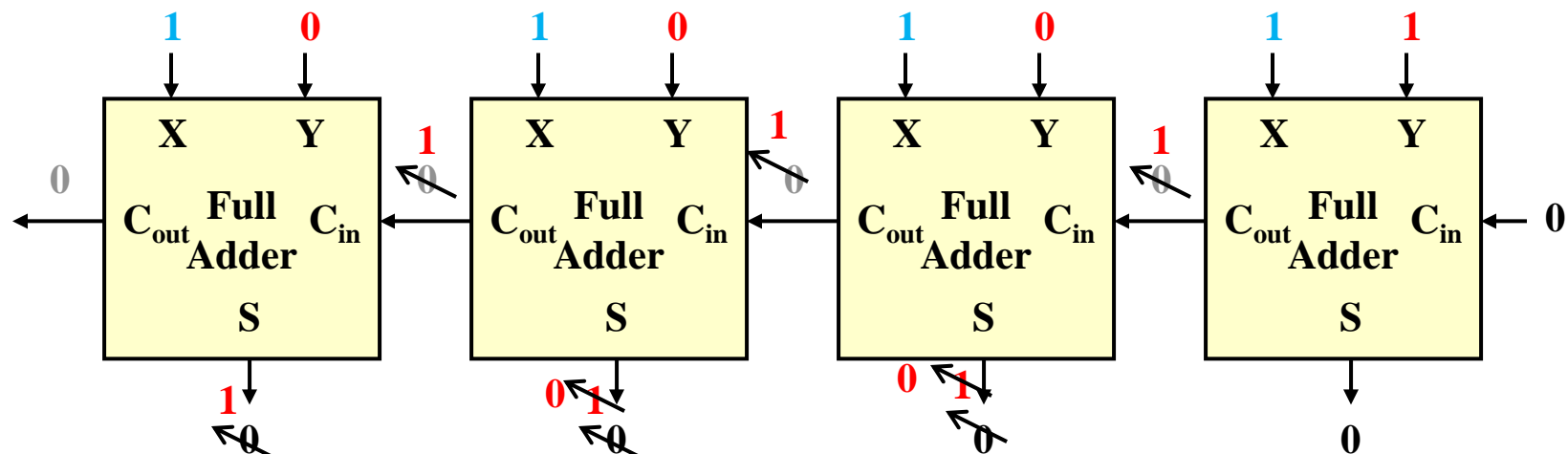

Timing


- Finally, all the adders are correct

New inputs:

$$\begin{array}{r}
 1 \quad \text{---} \\
 1111 = X \\
 + 0001 = Y \\
 \hline
 0000
 \end{array}$$

Time
4

Old inputs:

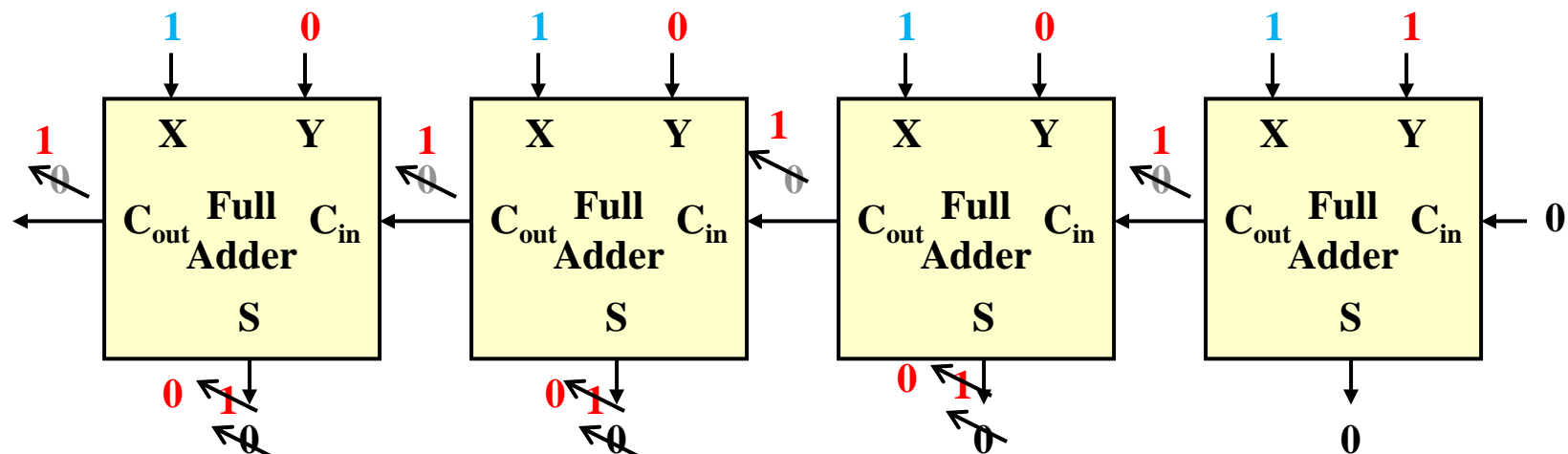


Sequential Devices (Registers)

- Combinational outputs are only a function of the current inputs
 - Outputs only depend on what the inputs are right now, not one second ago
 - This implies they have no “memory” (can't remember a value)
- Sequential logic devices provide the ability to retain or “remember” a value by itself (even after the input is changed or removed)
 - Usually have a controlling signal that indicates when the device should update the value it is remembering vs. when it should simply remember that value
 - This controlling signal is usually the “clock” signal



Clock Signal

 - Alternating high/low voltage pulse train
- Controls the ordering and timing of operations performed in the processor
- 1 cycle is usually measured from rising edge to rising edge
- Clock frequency = # of cycles per second (e.g. 2.8 GHz = $2.8 * 10^9$ cycles per second)



D Flip-Flop

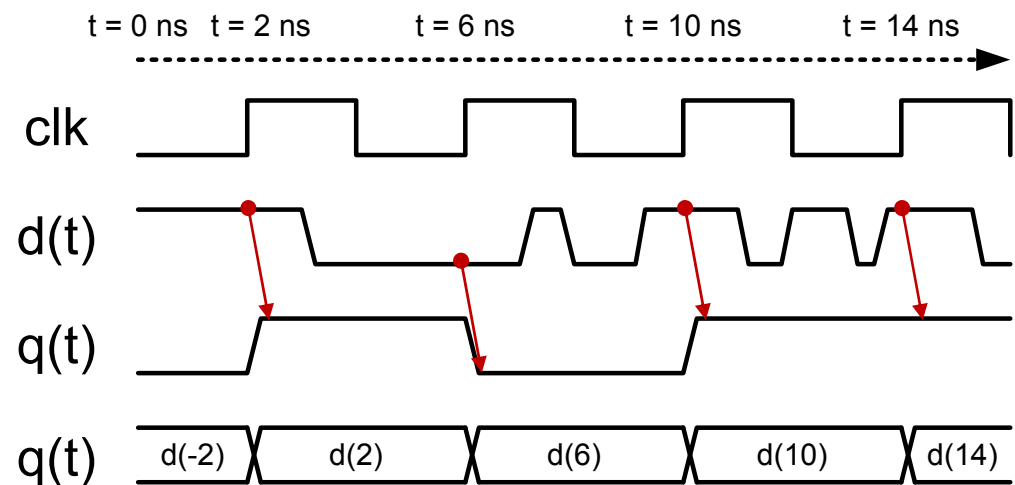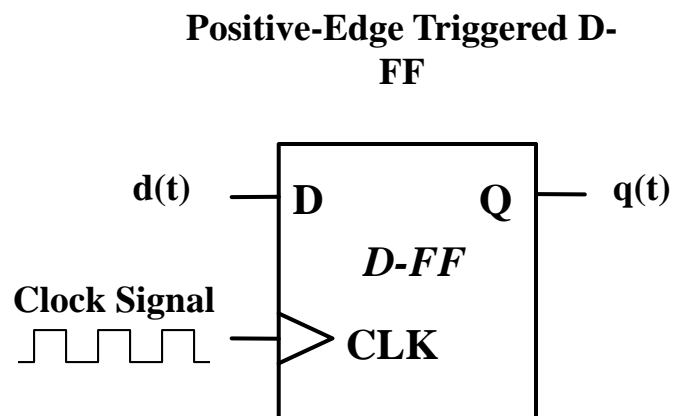
- Fundamental sequential building block
- q -output samples the d -input at the instant of the rising clock edge and then retains that value until the next clock edge



Positive-Edge Triggered D-FF

- Q looks at D only at the positive-edge

CLK	D	Q*
0	x	Q
1	x	Q
↑	0	0
↑	1	1

 


Q only samples D at the positive edges and then holds that value until the next edge

Registers

- A Register is a group of D-FFs tied to a common clock and clear (reset) input
 - Reset input allows register to be initialized to 0s
- Used to store multiple bit values on each clock cycle


CLK	/AR	D_i	Q_i^*
X	0	X	0
1,0	1	X	Q_i
↑	1	0	0
↑	1	1	1

 

4-bit Register

Registers

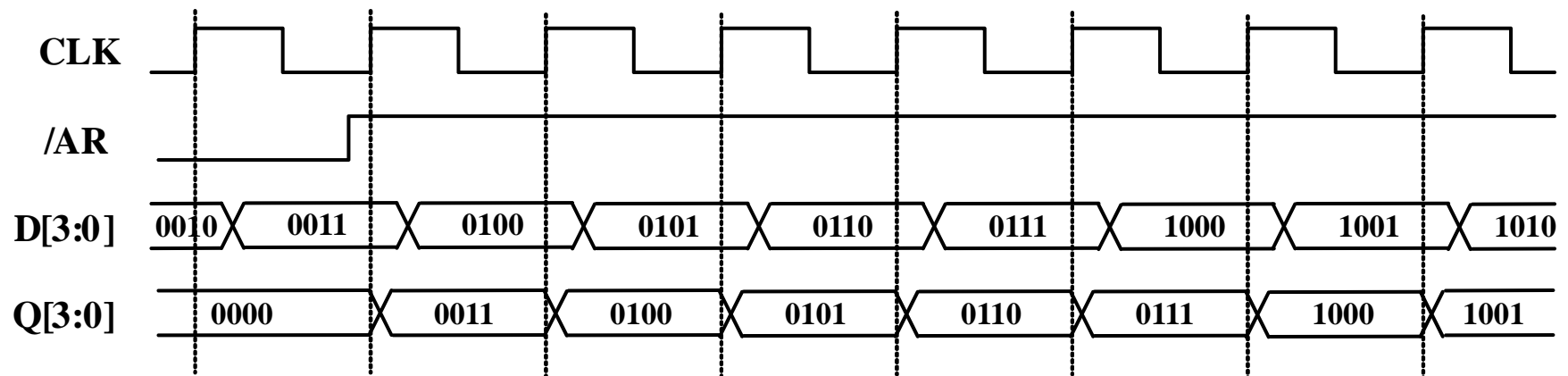
- Whatever the D value is at the clock edge, is sampled and passed to the Q output until the next clock edge




4-bit Register – On clock edge, D is passed to Q

Clocking Methodologies

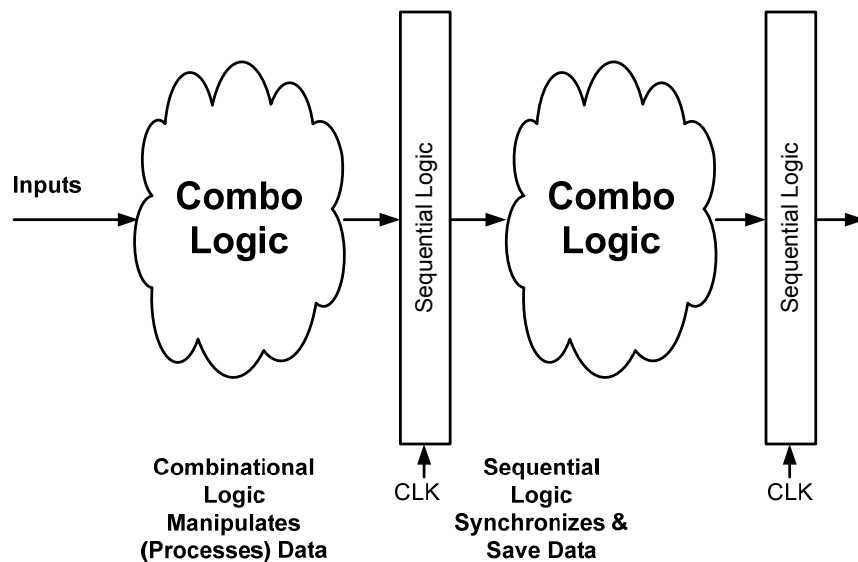- Typical designs use both combinational and sequential logic
 - Sequential logic: saves and synchronize data
 - Combinational logic: performs some operation on the data
- Can use feed-forward or feed-back methodology




Feed-forward Style

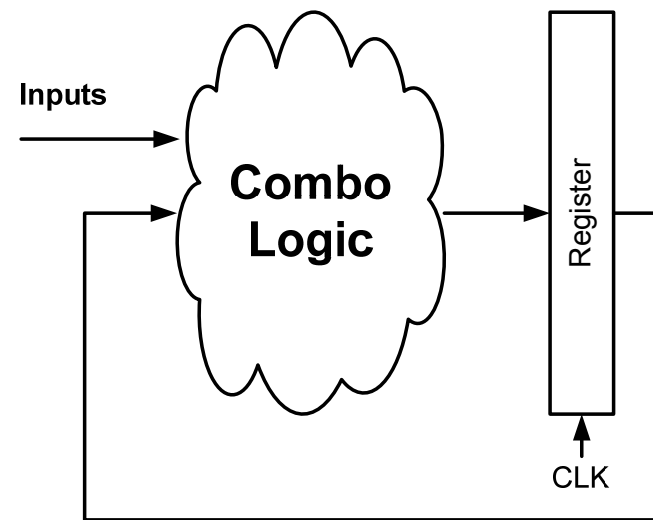

Feed-back Style

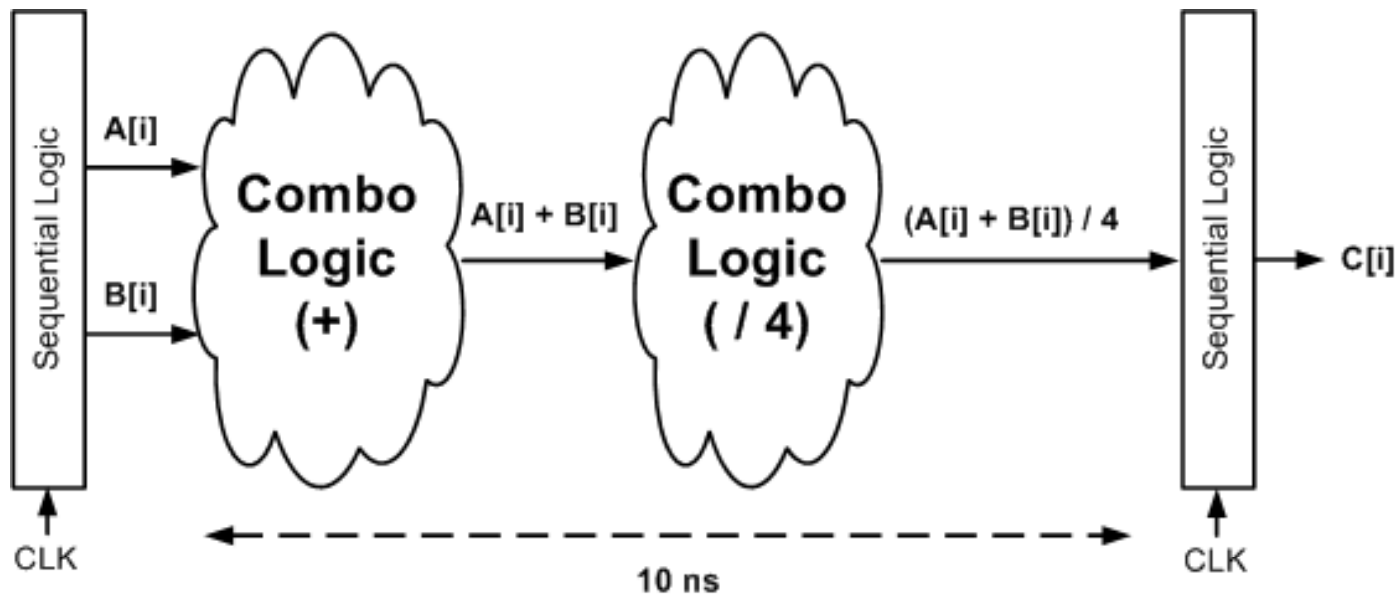Example


```
for(i=0; i < 100; i++)  
    C[i] = (A[i] + B[i]) / 4;
```



10 ns per input set = 1000 ns total

Feed-forward (Pipelining) Example

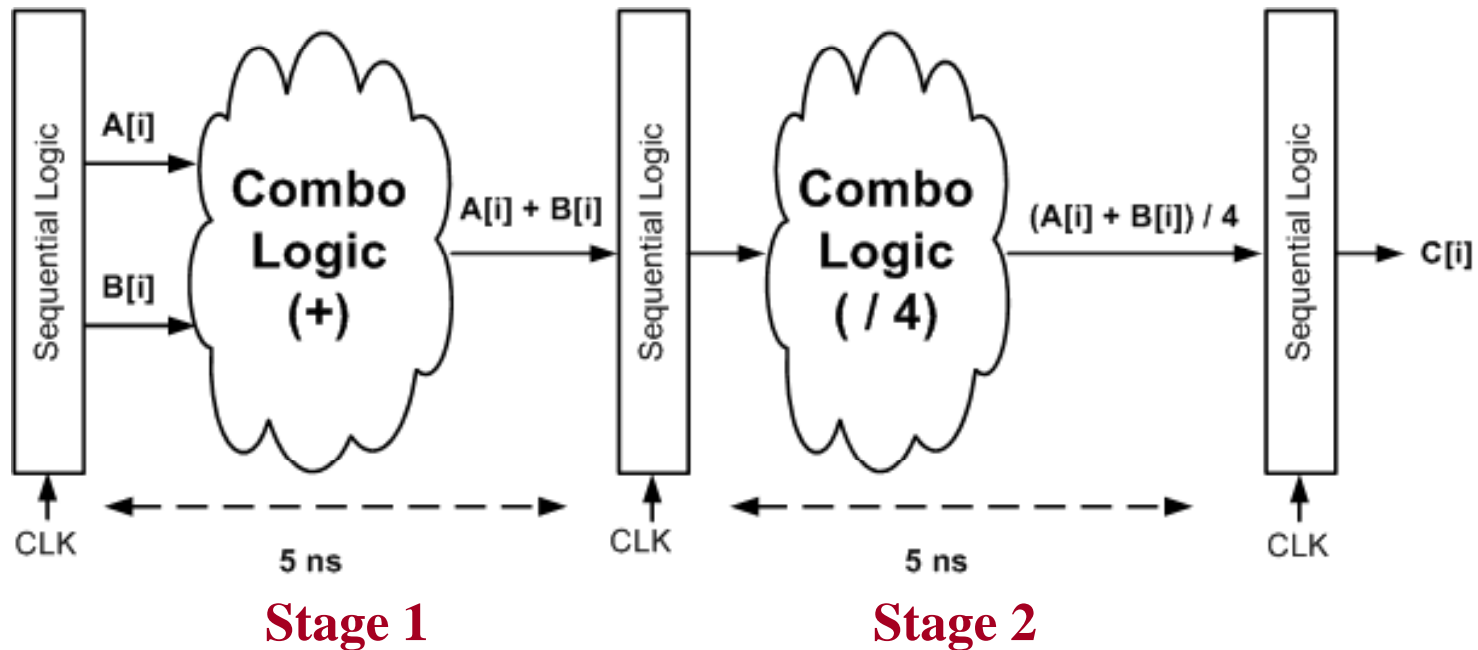
```
for(i=0; i < 100; i++)
  C[i] = (A[i] + B[i]) / 4;
```



	Stage 1	Stage 2
Clock 0	$A[0] + B[0]$	
Clock 1	$A[1] + B[1]$	$(A[0] + B[0]) / 4$
Clock 2	$A[2] + B[2]$	$(A[1] + B[1]) / 4$

Need for Registers

 - Provides separation between combinational functions
 - Without registers, fast signals could “catch-up” to data values in the next operation stage



Counter Example

